

# In-House Chip Design

**Pravin Zode**

Assistant Professor,  
Department of Electronics Engg.  
Yeshwantrao Chavan College of Engineering,  
Nagpur  
[ppzode@ycce.edu](mailto:ppzode@ycce.edu)

# Outline

- Introduction to Design
- Older Ways of design
- Modern Digital Design
- Programmable Logic Devices ( CPLD and FPGA)
- Demonstration of In-House Chip design




PAUL RAND

---

**"Design is so simple.  
That's why it is so  
complicated."**


# Older ways of Digital Design

 

- Discrete Logic : Can build small circuits only
- De-Morgan's Theorem :  
Theoretically we need only two input NAND and NOR gates
- Tedious , Expensive , slow, prone to wiring errors




# Early Digital Design using Gate Arrays

 

- Rows of Gates : Often Identical in nature
- Connected to form custom specific circuits
- Can be full custom, completed design from scratch
- Can be semi-custom ; customization on metal layer only
- Once fabricated , the design is fixed

# Modern Digital Designs

 


- Intel Core i7
- More than 3 billion transistors
- Very expensive to design
- Very expensive to manufacture
- Not viable unless the market is very large


# FPGA Vs Microcontroller

- With a microcontroller you write software
- The biggest limitation of software is that you can only do one thing at a time!
- With FPGAs you are not creating software
- You are designing the hardware!
- Instead of writing code to run on a fixed processor with fixed peripherals, you get to design your own circuit.
- If you really want to you can even create your very own processor and write software to run on it!
- A huge benefit of working with FPGAs is that every element of your design runs independently of each other
- That means one part of your design can be reading in some serial data, while another part is controlling a servo, while another is reading some sensors, and yet another is controlling a display

# System Design Flow

 


System design flow

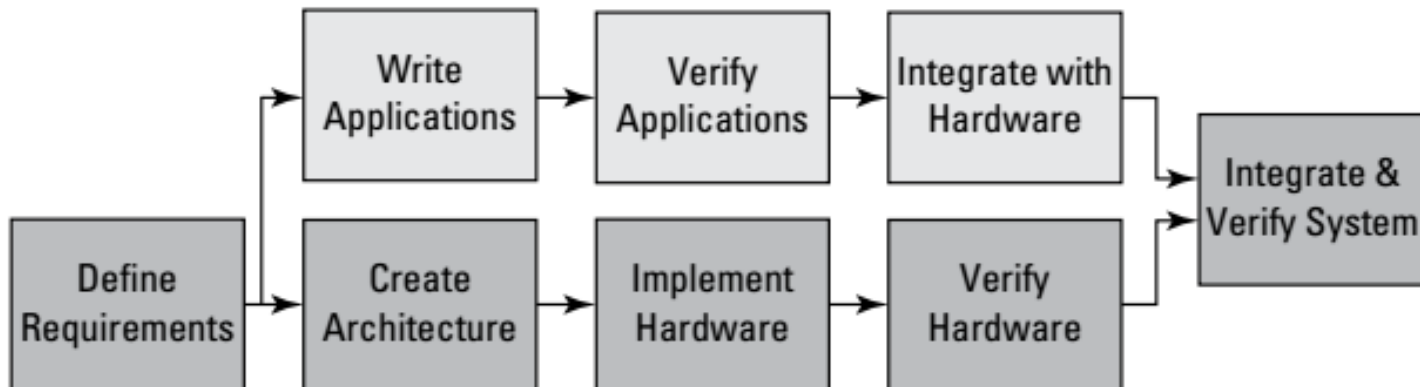


System design flow with the software application flow



# Middleware Design Flow

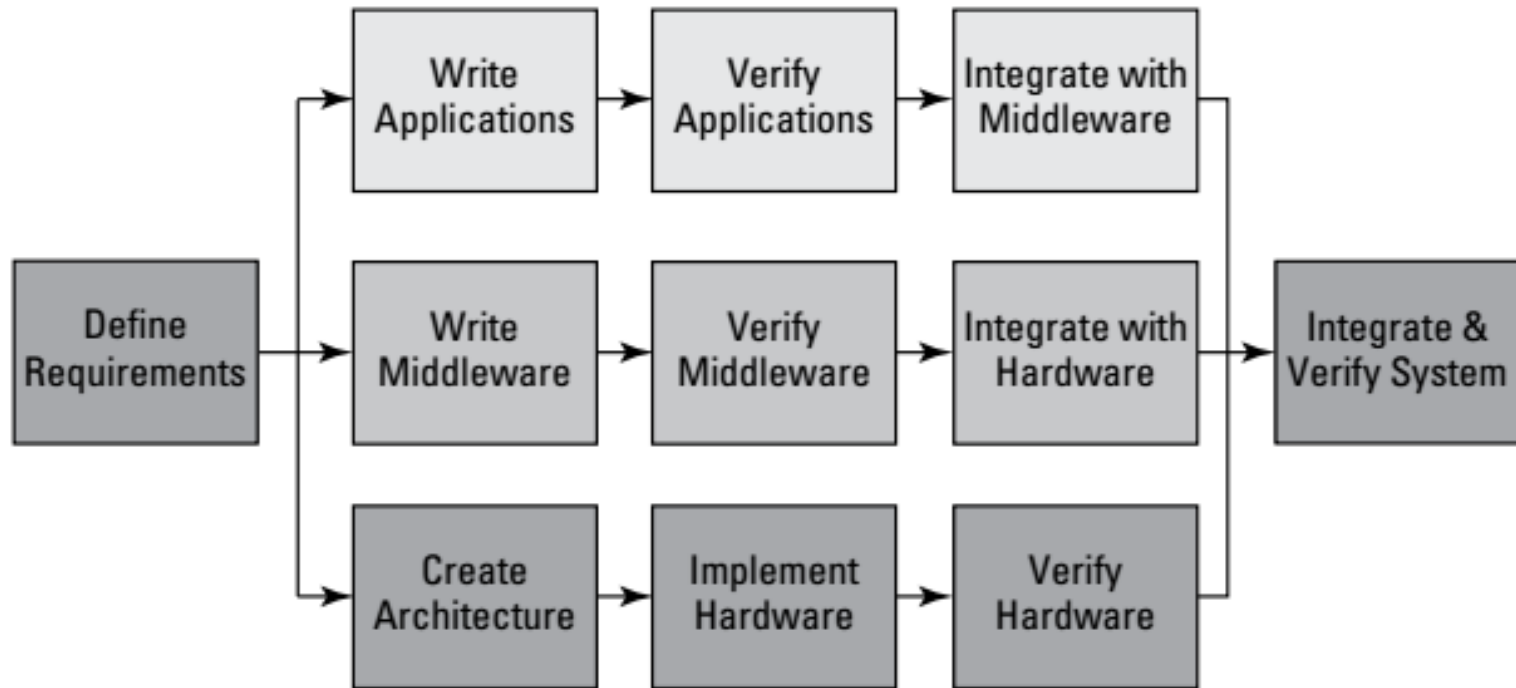


# Design Abstraction Level

 

# Design Abstraction Y Chart

Gajski-Kuhn Chart or Y-Chart

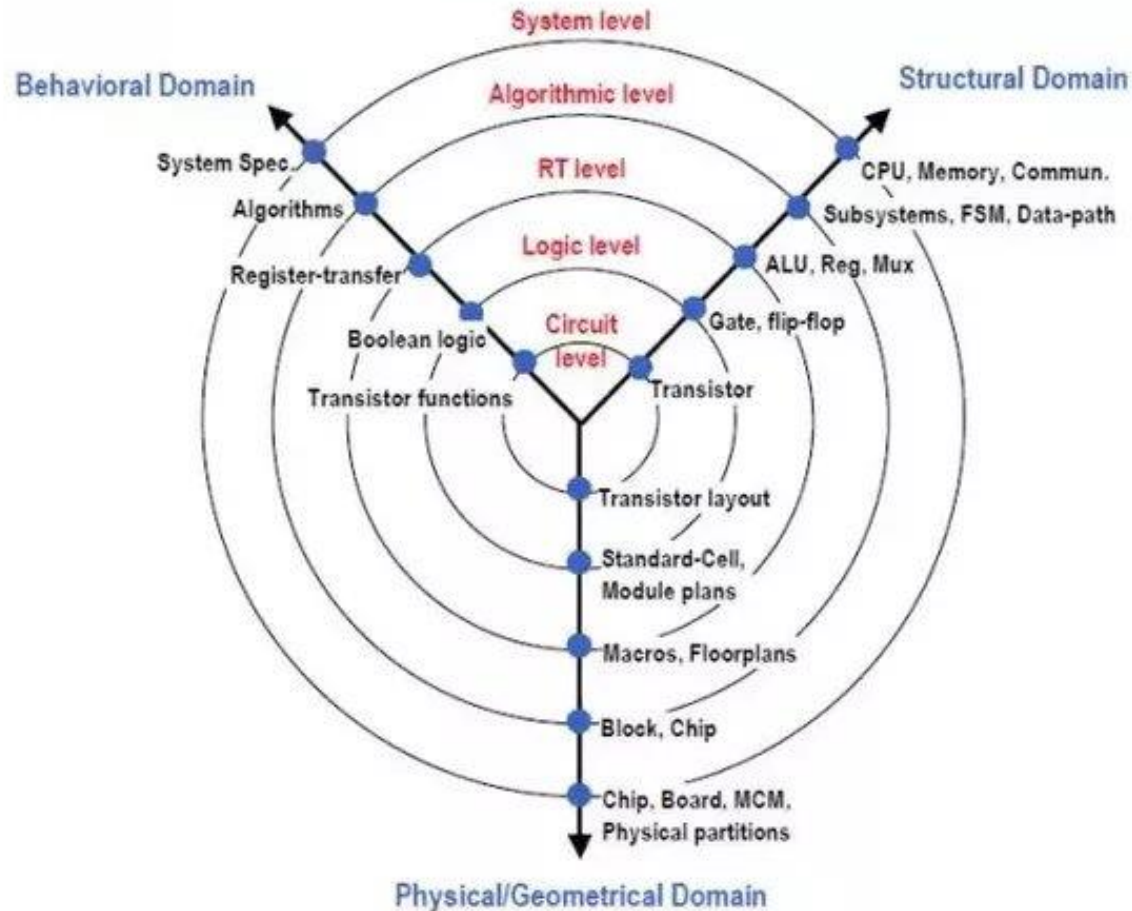

# Abstraction Levels in Hardware Design

## Levels of Abstraction:

- Behavioral Level: High-level algorithm description
- Register Transfer Level (RTL): Data transfer between registers
- Gate Level: Logic gates and flip-flops
- Physical Level: Layout and fabrication

# Register Transfer Level


**RTL** : Data transfers between registers and the operations performed on that data.

- **Register (R)**: A register is a small storage element that holds binary data (FF & Clock )
- **Transfer (T)**: Data is moved from one register to another via combinational logic (e.g., multiplexers, adders, ALUs)
- The movement occurs in a clock cycle and follows specific control signals.
- **Level (L)**: It describes how data moves between registers and how operations are performed, but it does not specify exact gate-level implementation.

# Key Components of RTL Design

- **Registers:** Storage elements (D Flip-Flops, Latches)
- **Combinational Logic:** Data processing (AND, OR, MUX, ALU)
- **Control Logic:** State machines, control signals
- **Clock and Reset:** Timing control

# Field Programmable Grid Array

 

- Combined idea of PLD and gate arrays
- First introduced by Xilinx in 1985
- Array of logic blocks
- Lot of programmable wiring
- Very flexible I/O interfacing
- Two dominant FPGA makers
  - Xilinx and Altera
- Other specialist makers
  - Actel and Lattice Logic


# Building blocks of FPGA

- A *register* remembers a piece of information until it is told to remember something else
- A *logic gate* performs simple logic operations on signals
- A *wire* connects these other pieces

– A wire



– A gate

 


– A register





 
# Older ways of Digital Design



- Based on Lookup Table ,most common 4 input
- Optional D-FF at the output
- 4-input LUT can implement any Boolean function
- Special circuits for cascading logic blocks ( carry chains )



# Programmable Routing

 


  - Wiring channels between rows and column
- These are programmable
- Each wiring segment can be connected in one or many ways


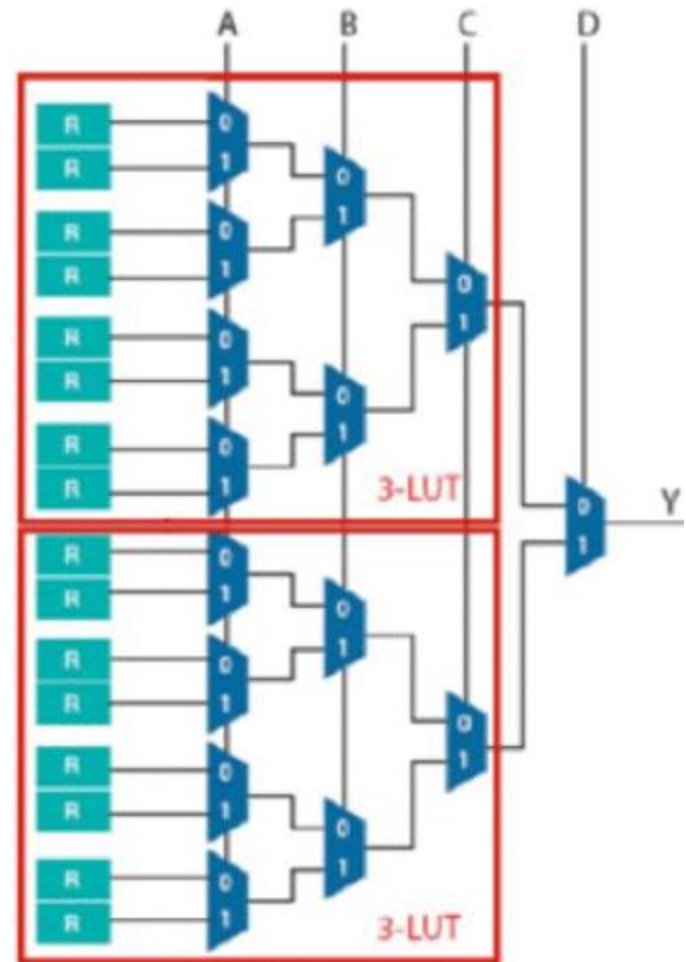
# Idea of configuring FPGA


- Programming FPGA is not same as microprocessor
- We download bitstream (not a program) to an FPGA
- Programming FPGA is known as configuration
- LUTs are configured to implement the Boolean logic




# Configuring the Routing of FPGA

- At each interconnect transistor switch OFF state
- Each switch is controlled by output of 1-bit configuration register
- Configuring the routing simply to put a '1' or '0' in register
- Bitstream is either stored on local flash memory or download via computer
- Configuration happens on power-up

Before Configuration

 

After Configuration

 

# Digital Designs

- Washing machine control using basic AND and NOT gates
- Basics of OR gate and its application in industrial control
- Basics of NOT gate and its application in an eight bit ones complement circuit
- Basic NOT gate and its application in fuel level indicator
- Seat belt warning system using basic AND and NOT gates
- Basics of AND gate and its application in car wiper control
- Water level control using basic AND and NOT gates
- Electronic lock using basic logic gates
- Universal NAND gate and its application in level monitoring in chemical plant
- Universal NOR gate and its application in automobile alarm system
- XOR gate and its application in staircase light control
- Majority circuit using basic logic gates
- Cockpit warning light control using basic logic gates
- Build your own combinational logic circuit using generalized simulator

# Low Fuel Warning System

# Low Fuel Warning System

In a vehicle, the fuel level sensor provides a signal indicating whether the fuel level is above a certain threshold. A NOT gate can be used to trigger a warning light when the fuel level is below this threshold.

## Inputs:

- **A:** Binary input signal from the fuel level sensor (1 if fuel level is above threshold, 0 if below).

## Output:

- **Y:** Binary output signal to the warning light (1 to turn on the warning light, 0 to turn it off).

# Industry Emergency Indicator



# Emergency Stop System

**Emergency Stop System:** In an industrial environment, multiple emergency stop buttons are placed at different locations. Pressing any one of these buttons should stop the machinery to ensure safety.

## Inputs:

- A: Signal from emergency stop button 1.
- B: Signal from emergency stop button 2.

## Output:

- Y: Signal to stop the machinery (1 if any emergency stop button is pressed).

## OR Gate:

- Output Y will be high (1) if either A or B is high (1), stopping the machinery.

# Car Wiper Control System

# Car Wiper Control System

Car wiper control system to ensure the wipers operate only when both the ignition is on and the wiper switch is activated.

## Inputs:

- **A:** Binary input signal from the ignition switch (1 if ignition is on, 0 if off).
- **B:** Binary input signal from the wiper switch (1 if wiper switch is on, 0 if off).

## Output:

- **Y:** Binary output signal to the wiper motor (1 to activate the wipers, 0 to deactivate them).

# Water Level Control System

# Water Level Control System

The water level control system should ensure that the water pump operates only when the water level is below a certain threshold and the system is enabled. Once the water reaches the desired level, the pump should automatically turn off.

## Inputs:

**L:** Binary input signal from the low water level sensor (1 if water is below threshold, 0 otherwise).

**H:** Binary input signal from the high water level sensor (1 if water is at or above desired level, 0 otherwise).

**E:** Binary input signal for enabling the system (1 if system is enabled, 0 otherwise).

## Outputs:


**P:** Binary output signal controlling the water pump (1 to turn on the pump, 0 to turn it off).

# Water Level Control System

Low Level (L)	High Level (H)	System Enabled (E)	NOT H	Pump (P = NOT H AND L AND E)
0	0	0	1	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	0
1	1	1	0	0



# **Seat Belt Warning Indicator**

# Seat Belt Indicator

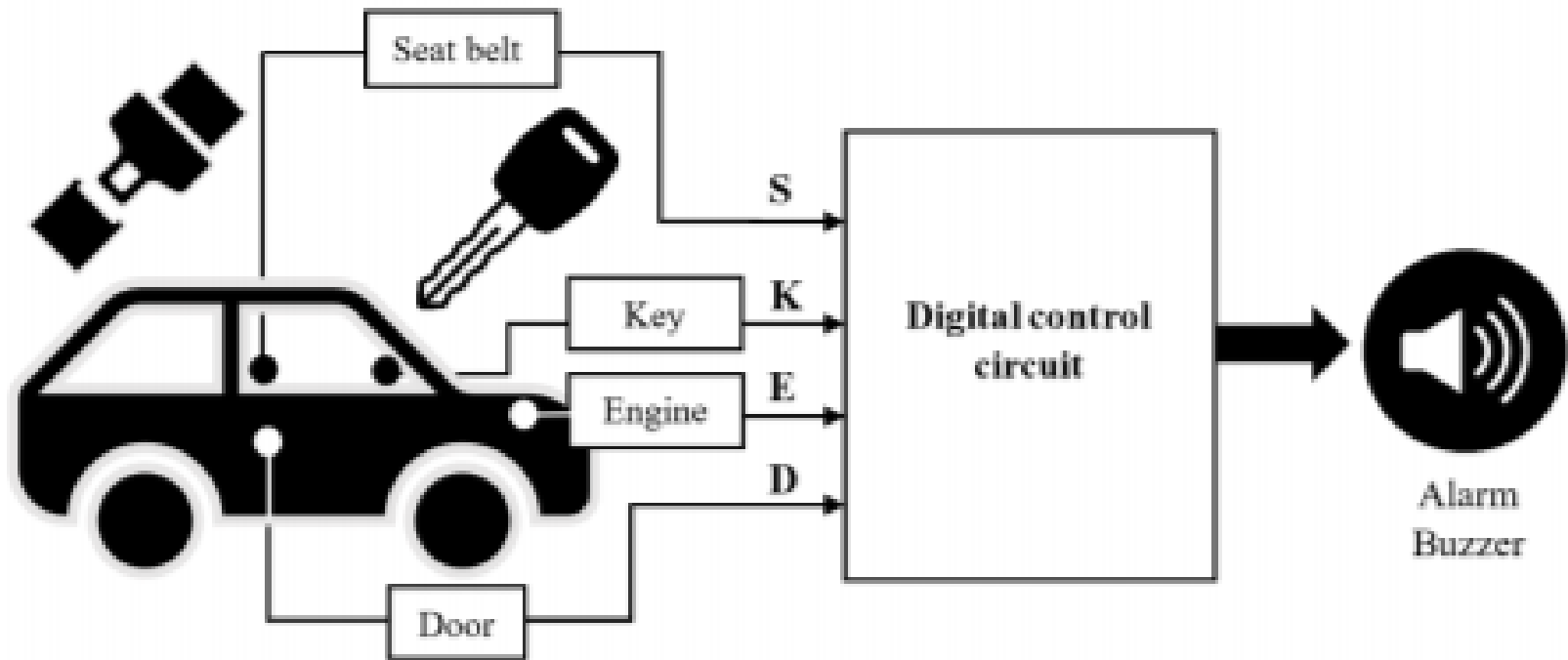



# Seat Belt Indicator

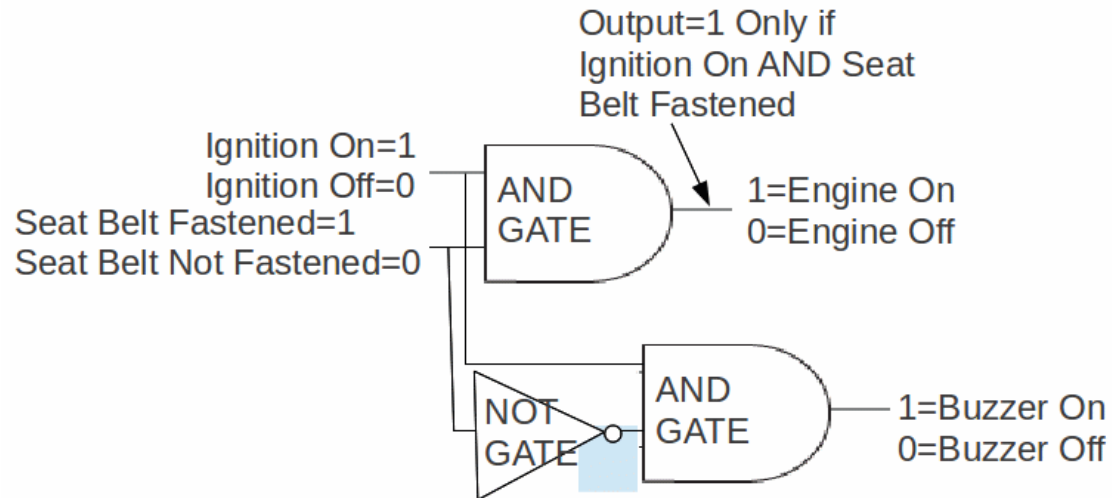 

# Electronic Lock

# Electronic Lock

The electronic lock should only unlock when a specific combination of inputs is provided.

The lock should unlock only when  $A=1$ ,  $B=0$ , and  $C=1$ .

# Washing Machine Control

# Washing Machine Control System

## Problem Definition

The washing machine should only start its operation when the following conditions are simultaneously satisfied:

- Water is present
- Laundry is loaded
- The lid is closed

# Solution : Washing Machine Control System

## Inputs:

- **X**: Binary input signal indicating the presence of water (1 if water is present, 0 otherwise).
- **Y**: Binary input signal indicating the presence of laundry (1 if laundry is loaded, 0 otherwise).
- **Z**: Binary input signal indicating whether the lid is closed (1 if the lid is closed, 0 otherwise).

## Output:

- **C**: Binary output signal controlling the washing machine (0 to start the machine, 1 to stop the machine).

# Logic Design : Washing Machine Control System

## **AND Gate 1:**

- Inputs: X, Y
- Output: A (X AND Y)
- Description: This gate ensures that both water and laundry are present.

## **AND Gate 2:**

- Inputs: A, Z
- Output: B (A AND Z)
- Description: This gate ensures that the machine will only consider starting if both the previous condition (water and laundry present) is met and the lid is closed.

## **NOT Gate:**

- Input: B
- Output: C (NOT B)
- Description: This gate inverts the signal, so the washing machine starts (C=0) only if all conditions are satisfied (B=1).

# Logic Design : Washing Machine Control System

<b>X</b> <b>Water</b>	<b>Y</b> <b>Laundry</b>	<b>Z</b> <b>Lid</b>	<b>A</b> <b>(X AND Y)</b>	<b>B</b> <b>(A AND Z)</b>	<b>C</b> <b>(NOT B)</b>
0	0	0	0	0	1
0	0	1	0	0	1
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	0	1
1	0	1	0	0	1
1	1	0	1	0	1
1	1	1	1	1	0

- The designed control circuit ensures that the washing machine operates only when all required conditions (**water present, laundry loaded, lid closed**) are met.
- This prevents the machine from starting under unsafe or incorrect conditions, thereby **ensuring efficient and safe operation**.




# **Majority Circuit (Electronic Voting Machine)**

# Majority Circuit


A majority circuit outputs true (1) if the majority of the inputs are true (1). For three inputs, the output should be true if at least two of the three inputs are true. ( Voting Machine/Committee Decisions/Fault Tolerant Systems/ etc..... )

A	B	C	A AND B	A AND C	B AND C	Y (Majority)
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	0	0	0
1	0	1	0	1	0	1
1	1	0	1	0	0	1
1	1	1	1	1	1	1

# CPLD Development Board

 

# CPLD Development Board

 

# HDL Programming

# Verilog Code NOT Gate

## Verilog Code

```
module inverter ( input wire a, output wire y );  
    assign y = ~a;  
endmodule
```

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity inverter is  
    Port (  
        a : in STD_LOGIC;  -- Input signal  
        y : out STD_LOGIC  -- Output signal  
    );  
end inverter;  
  
architecture Behavioral of inverter is  
begin  
    y <= not a; -- Output is the negation  
                (inversion) of the input  
end Behavioral;
```

## VHDL Code

# Slower Clock

```
1  module slower_clock(input clk, output reg clkOutput);
2
3  reg [22:0] counter;
4
5  always @(posedge clk)
6      if(counter==5000000) counter <= 0; else counter <= counter+1;
7
8  always @(posedge clk)
9      if(counter==5000000)
10         begin
11             clkOutput <= ~clkOutput;
12         end
13  endmodule
```

LED is blinking at 5Hz  
clock pins (12, 14, 62)

```
1  module ledblink(clk,led);
2  input clk; output led; reg led;
3  reg[23:0] cnt;
4  always @(posedge clk) begin cnt<= cnt + 1'b1; led<=cnt[23];
5  end
6  endmodule
```

# Fine Tuning with PWM

```
1  module LED_PWM(clk, PWM_input, LED);
2  input clk;
3  input [3:0] PWM_input;    // 16 intensity levels
4  output LED;
5
6  reg [4:0] PWM;
7  always @(posedge clk) PWM <= PWM[3:0] + PWM_input;
8
9  assign LED = PWM[4];
10 endmodule

1  module LEDglow(clk, LED);
2  input clk;
3  output LED;
4
5  reg [23:0] cnt;
6  always @(posedge clk) cnt <= cnt+1;
7
8  reg [4:0] PWM;
9  wire [3:0] intensity = cnt[23] ? cnt[22:19] : ~cnt[22:19];
10 // ramp the intensity up and down
11 always @(posedge clk) PWM <= PWM[3:0] + intensity;
12
13 assign LED = PWM[4];
14 endmodule
```



# Verilog Code for LED Blinking

```
module counter(clk, out);  
    input clk;    // Clock input  
    output out;   // Output signal  
    reg out;      // Register for the output  
    reg [23:0] count; // 24-bit register for the counter  
    // Always block triggered on the positive edge of the clock  
    always @(posedge clk) begin  
        count <= count + 1'b1; // Increment the counter by 1  
        out <= count[23];    // Assign the 24th bit of the counter to the output  
    end  
endmodule
```

# VHDL Code for LED Blinking

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;


entity counter is
    Port (
        clk : in STD_LOGIC; -- Clock input
        out : out STD_LOGIC -- Output signal
    );
end counter;

architecture Behavioral of counter is
    signal count : STD_LOGIC_VECTOR(23 downto 0) := (others => '0'); -- 24-bit counter signal
begin
    process(clk)
    begin
        if rising_edge(clk) then
            count <= count + 1;      -- Increment the counter
            out <= count(23);        -- Assign the 24th bit of the counter to the output
        end if;
    end process;
end Behavioral;
```

# Music Generation

# Music

- Simple beeps
- Sirens
- Notes
- Tune

 

# Music: Simple Beep (Verilog)

```
module music(clk, speaker);  
input clk;  
output speaker;  
  
// first create a 16bit binary counter  
reg [15:0] counter;  
always @(posedge clk) counter <= counter+1;  
  
// and use the most significant bit (MSB) of the counter to drive  
the speaker  
assign speaker = counter[15];  
endmodule
```

# Music: Simple Beep (VHDL)

entity music is

Port (

clk : in STD\_LOGIC; -- Clock input

speaker : out STD\_LOGIC -- Speaker output

);

end music;

architecture Behavioral of music is

signal counter : STD\_LOGIC\_VECTOR(15 downto 0) := (others => '0');

begin

process(clk)

begin

if rising\_edge(clk) then

counter <= counter + 1;

end if;

end process;

speaker <= counter(15);

end Behavioral;

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

use IEEE.STD\_LOGIC\_ARITH.ALL;

use IEEE.STD\_LOGIC\_UNSIGNED.ALL;


# Classroom and Feedback



Pre Course  
Delivery  
Feedback



Google  
Classroom

 

**Thank you !**

**Happy Learning**