

Verilog HDL: Structural Design

Pravin Zode

Outline

- Structural Design
- Top-Down Design Methodology
- Example : Adder Circuit


Structural Design

- Structural design partitioning for better organization and reuse
- Modular approach improves design clarity and maintainability.
- Simplifies debugging and verification by dividing the design into smaller components


Top-Down Design Methodology

- **Top-Down Design Methodology**

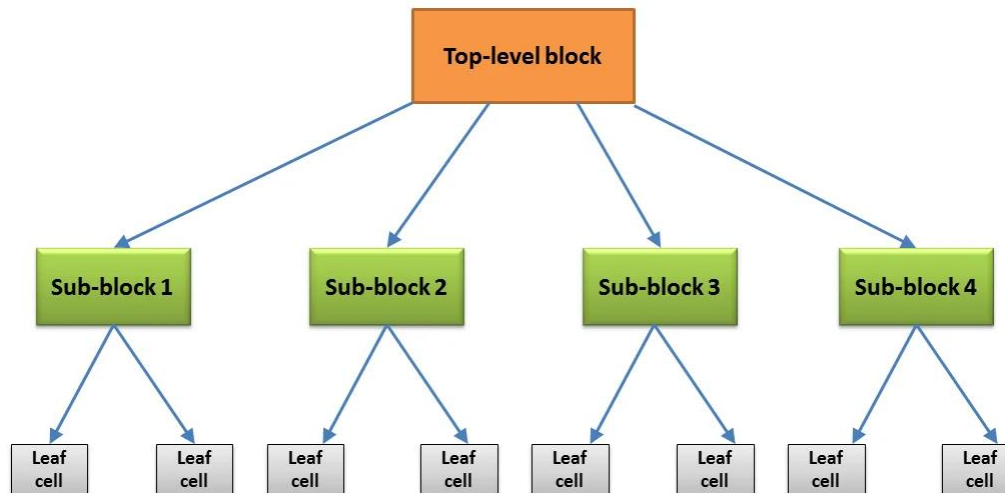- Starts with the top-level block and identifies required sub-blocks
- Sub-blocks are further divided until leaf cells are reached
- Leaf cells are the smallest units that cannot be further divided
- Helps in systematic partitioning and abstraction.




Top-Down Design Methodology

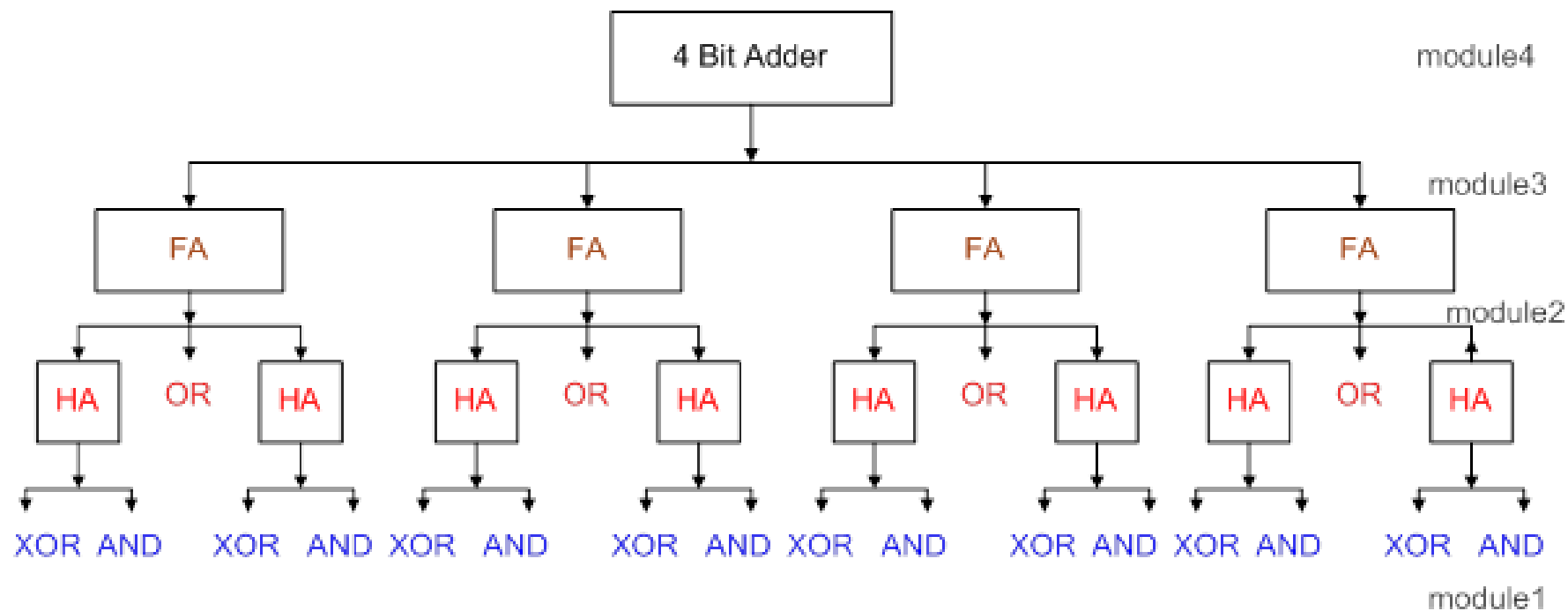

Bottom-Up Design Methodology

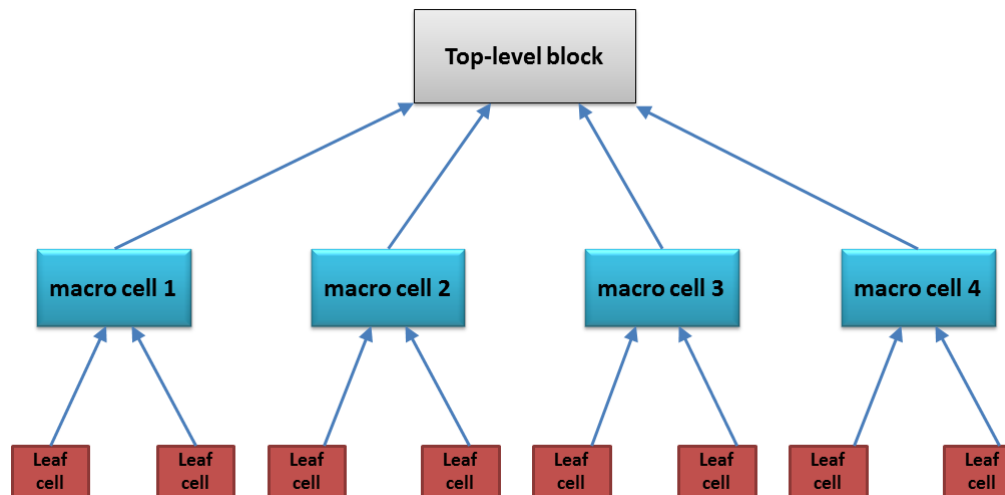- Begins with available building blocks
- Smaller blocks are combined to form larger blocks
- Continues until the top-level block is constructed
- Useful when pre-designed components are available.



Mixed Design Methodology

Combination of Top-Down and Bottom-Up Approaches

- Design architects define the top-level specifications
- Logic designers break down the functionality into blocks and sub-blocks
- Circuit designers optimize leaf cells and build higher-level circuits
- The process meets at an intermediate point, integrating both approaches
- Ensures efficient design, optimization, and reusability

Verilog Gates

Name	Description	Usage
and	$f = (a \cdot b \cdots)$	and (f, a, b, \dots)
nand	$f = \overline{(a \cdot b \cdots)}$	nand (f, a, b, \dots)
or	$f = (a + b + \cdots)$	or (f, a, b, \dots)
nor	$f = \overline{(a + b + \cdots)}$	nor (f, a, b, \dots)
xor	$f = (a \oplus b \oplus \cdots)$	xor (f, a, b, \dots)
xnor	$f = (a \odot b \odot \cdots)$	xnor (f, a, b, \dots)
not	$f = \bar{a}$	not (f, a)
buf	$f = a$	buf (f, a)
notif0	$f = (!e ? \bar{a} : 'bz)$	notif0 (f, a, e)
notif1	$f = (e ? \bar{a} : 'bz)$	notif1 (f, a, e)
bufif0	$f = (!e ? a : 'bz)$	bufif0 (f, a, e)
bufif1	$f = (e ? a : 'bz)$	bufif1 (f, a, e)

Structural Description Adder

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  xor (s, x, y, Cin);  
  and (z1, x, y);  
  and (z2, x, Cin);  
  and (z3, y, Cin);  
  or (Cout, z1, z2, z3);  
  
endmodule
```

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  xor (s, x, y, Cin);  
  and (z1, x, y),  
      (z2, x, Cin),  
      (z3, y, Cin);  
  or (Cout, z1, z2, z3);  
  
endmodule
```


Structural Description Adder

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  xor (s, x, y, Cin);  
  and (z1, x, y);  
  and (z2, x, Cin);  
  and (z3, y, Cin);  
  or (Cout, z1, z2, z3);  
  
endmodule
```

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  wire z1, z2, z3, z4;  
  
  and And1 (z1, x, y);  
  and And2 (z2, x, Cin);  
  and And3 (z3, y, Cin);  
  or Or1 (Cout, z1, z2, z3);  
  xor Xor1 (z4, x, y);  
  xor Xor2 (s, z4, Cin);  
  
endmodule
```

Port Mapping

Explicit Port Mapping

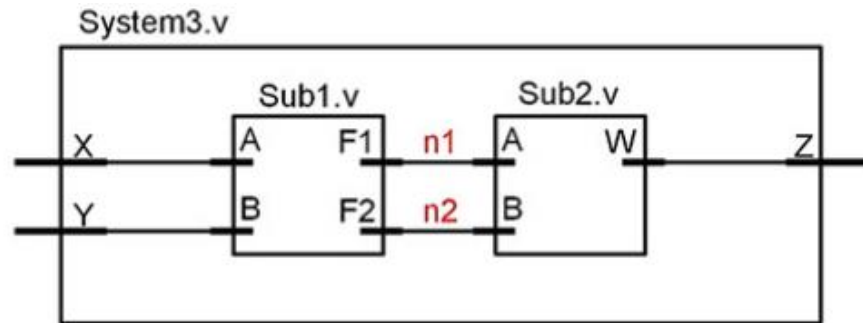

```
module Sub1 (output wire F1, F2,  
             input wire A, B);  
  
    // behavior here...  
  
endmodule
```

```
module Sub2 (output wire W,  
             input wire A, B);  
  
    // behavior here...  
  
endmodule
```


```
module System3 (output wire Z,  
                input wire X, Y);  
  
    wire n1, n2;  
  
    Sub1 U0 (.F1(n1), .F2(n2), .A(X), .B(Y));  
    Sub2 U1 (.W(Z), .A(n1), .B(n2));  
  
endmodule
```

The lower-level port name is explicitly listed (preceded by a period).


The signal being connected to the lower-level port is listed inside of parenthesis.

Port Mapping

Positional Port Mapping

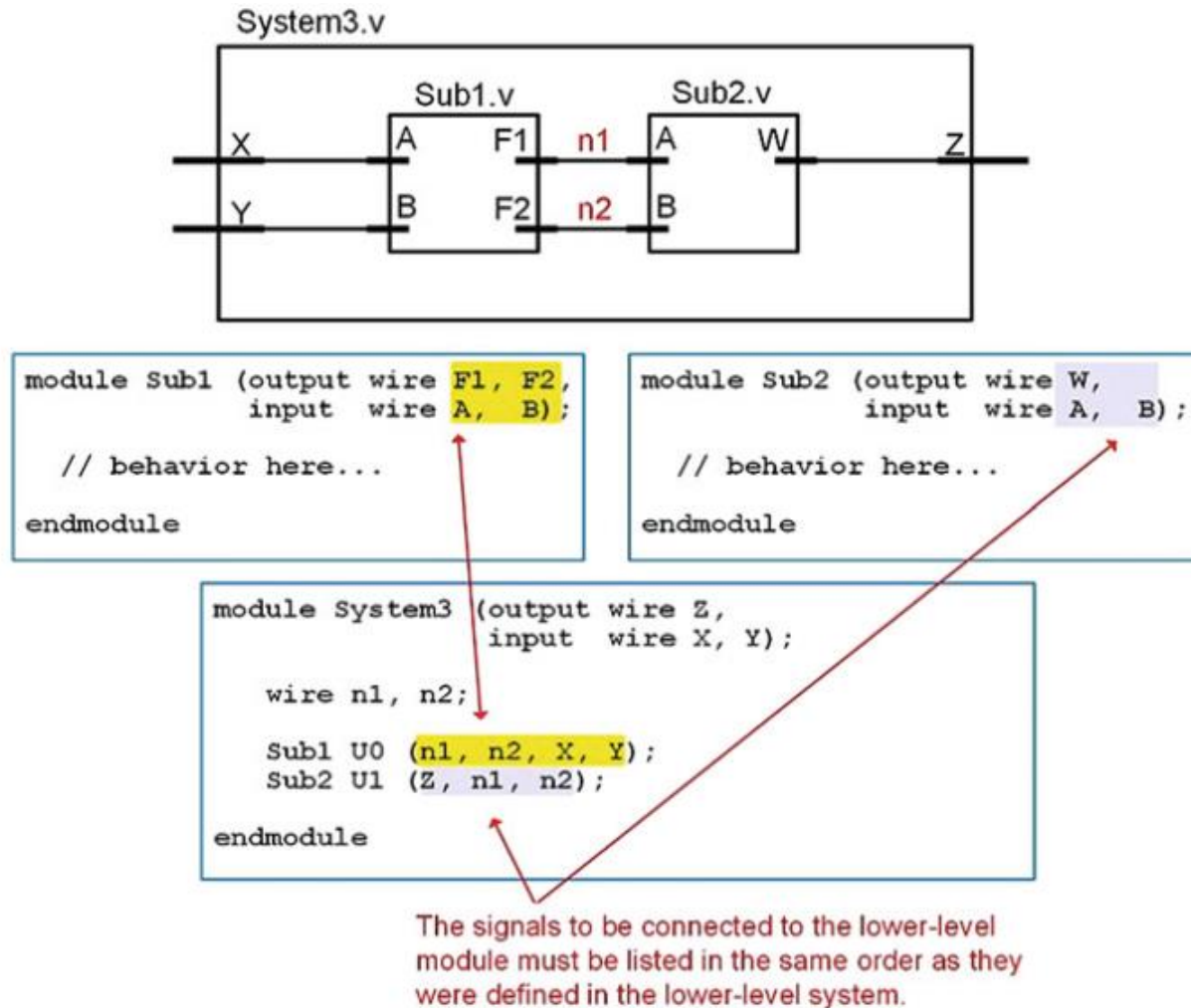

Full Adder

 

```
module full_adder(sum,carry,x,y,z)
    input x,y,z;
    output sum,carry;

    half_adder ha1(.s(s1), .c(c1), .a(x), .b(y));
    //half_adder ha1(s1,c1,a,b);//above method is good
    half_adder ha2(.s(sum), .c(c2), .a(s1), .b(z));
    or o1(.c(carry), .a(c1), .b(c2));
endmodule
```

Full Adder

```
module adder4 (carryin, x3, x2, x1, x0, y3, y2, y1, y0, s3, s2, s1, s0, carryout);  
  input carryin, x3, x2, x1, x0, y3, y2, y1, y0;  
  output s3, s2, s1, s0, carryout;
```

```
  fulladd stage0 (carryin, x0, y0, s0, c1);  
  fulladd stage1 (c1, x1, y1, s1, c2);  
  fulladd stage2 (c2, x2, y2, s2, c3);  
  fulladd stage3 (c3, x3, y3, s3, carryout);
```


```
endmodule
```

```
module fulladd (Cin, x, y, s, Cout);  
  input Cin, x, y;  
  output s, Cout;  
  
  assign s = x ^ y ^ Cin;  
  assign Cout = (x & y) | (x & Cin) | (y & Cin);
```

```
endmodule
```

Full Adder
 
```
module adder4 (carryin, X, Y, S, carryout);  
    input carryin;  
    input [3:0] X, Y;  
    output [3:0] S;  
    output carryout;  
    wire [3:1] C;  
  
    fulladd stage0 (carryin, X[0], Y[0], S[0], C[1]);  
    fulladd stage1 (C[1], X[1], Y[1], S[1], C[2]);  
    fulladd stage2 (C[2], X[2], Y[2], S[2], C[3]);  
    fulladd stage3 (C[3], X[3], Y[3], S[3], carryout);  
  
endmodule
```



Thank you !

Happy Learning