

Assignment-02 (Conditional Operator)

Write Verilog code using conditional operator

1. 4:1 multiplexer
2. 7 segment display decoder
3. 4:2 Binary Encoder
4. 1:4 Demultiplexer